

# CPSC 359 Assignment 2: Gray Code Up/Down Counter

Kell Larson 30056026

## 1. The Problem:

Adding or subtracting gray code values when a button is pushed, with an enable/disable button for the adder/subtractor logic

## 2. Variable Symbolization:

Input Variables:

D: direction

E: enable

Output Variables:

G1, G2, G3: Gray code bits, with G1 being the least significant, G3 being the most, and G2 being in the middle.

Flip Flops: A,B,C

## 3. State Diagram:

Present state			Next state, E = 1												Next state, E = 0, D = x					
A	B	C	D = 0						D = 1						Output					
			A	B	C	Output			A	B	C	Output			A	B	C	G1	G2	G3
						G1	G2	G3				G1	G2	G3						
0	0	0	0	0	1	0	0	1	1	1	1	1	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1	1	0	0	0	0	0	0	0	0	1	0	0	1
0	1	0	0	1	1	0	1	0	0	0	1	0	0	1	0	1	0	0	1	1
0	1	1	1	0	0	1	1	0	0	1	0	0	1	1	0	1	1	0	1	0
1	0	0	1	0	1	1	1	1	0	1	1	0	1	0	1	0	0	1	1	0
1	0	1	1	1	0	1	0	1	1	0	0	1	1	0	1	0	1	1	1	1
1	1	0	1	1	1	1	0	0	1	0	1	1	1	1	1	1	0	1	0	1
1	1	1	0	0	0	0	0	0	1	1	0	1	0	1	1	1	1	1	0	0

## 4. Input and Output Variables:

Input Variables:

Direction: whether to add or subtract the gray code

Enable: whether or not to add or subtract the gray code

Output Variables: 3-bit gray code

Flip-Flops required: 3 JK flip-flops

## CPSC 359 Assignment 2: Gray Code Up/Down Counter

Kell Larson 30056026

### 5. Excitation Table:

Combinational Circuit Inputs					Next state			Combinational Circuit Outputs					
Present state			Input					Flip-Flop Inputs					
A	B	C	D	E	A	B	C	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	x	0	0	0	0	0	0	0	0	0	0
0	0	1	x	0	0	0	1	0	0	0	0	0	0
0	1	0	x	0	0	1	0	0	0	0	0	0	0
0	1	1	x	0	0	1	1	0	0	0	0	0	0
1	0	0	x	0	1	0	0	0	0	0	0	0	0
1	0	1	x	0	1	0	1	0	0	0	0	0	0
1	1	0	x	0	1	1	0	0	0	0	0	0	0
1	1	1	x	0	1	1	1	0	0	0	0	0	0
0	0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	1	0	1	0	0	0	1	1	1	1
0	1	0	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	1	1	0	0	1	1	1	1	1	1
1	0	0	0	1	1	0	1	0	0	0	0	1	1
1	0	1	0	1	1	1	0	0	0	1	1	1	1
1	1	0	0	1	1	1	1	0	0	0	0	1	1
1	1	1	0	1	0	0	0	1	1	1	1	1	1
0	0	0	1	1	1	1	1	1	1	1	1	1	1
0	0	1	1	1	0	0	0	0	0	0	0	1	1
0	1	0	1	1	0	0	1	0	0	1	1	1	1
0	1	1	1	1	0	1	0	0	0	0	0	1	1
1	0	0	1	1	0	1	1	1	1	1	1	1	1
1	0	1	1	1	1	0	0	0	0	0	0	1	1
1	1	0	1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	1	1	0	0	0	0	0	1	1

### 6. Circuit Output Functions:

Please see handwritten page 1 for circuit output functions.

### 7. Flip-flop Input Functions:

Please see handwritten page 2 and 3 for flip flop input functions.

### 8. Implementation of Logic Diagrams:

Please see handwritten page 4 of the report for implemented logic diagrams.

# CPSC 359 Assignment 2: Gray Code Up/Down Counter

Kell Larson 30056026

## 1. Bonus Input and Output Variables:

Input Variables:

Direction: whether to add or subtract the gray code

Enable: whether or not to add or subtract the gray code

Output Variables: 3-bit gray code

Flip-Flops required: 3 T flip-flops

## 2. Bonus Excitation Table:

Combinational Circuit Inputs					Next state			Combinational Circuit Outputs		
Present state			Input					Flip-Flop Inputs		
A	B	C	D	E	A	B	C	T <sub>A</sub>	T <sub>B</sub>	T <sub>C</sub>
0	0	0	x	0	0	0	0	0	0	0
0	0	1	x	0	0	0	1	0	0	0
0	1	0	x	0	0	1	0	0	0	0
0	1	1	x	0	0	1	1	0	0	0
1	0	0	x	0	1	0	0	0	0	0
1	0	1	x	0	1	0	1	0	0	0
1	1	0	x	0	1	1	0	0	0	0
1	1	1	x	0	1	1	1	0	0	0
0	0	0	0	1	0	0	1	0	0	1
0	0	1	0	1	0	1	0	0	1	1
0	1	0	0	1	0	1	1	0	0	1
0	1	1	0	1	1	0	0	1	1	1
1	0	0	0	1	1	0	1	0	0	1
1	0	1	0	1	1	1	0	0	1	1
1	1	0	0	1	1	1	1	0	0	1
1	1	1	0	1	0	0	0	1	1	1
0	0	0	1	1	1	1	1	1	1	1
0	0	1	1	1	0	0	0	0	0	1
0	1	0	1	1	0	0	1	0	1	1
0	1	1	1	1	0	1	0	0	0	1
1	0	0	1	1	0	1	1	1	1	1
1	0	1	1	1	1	0	0	0	0	1
1	1	0	1	1	1	0	1	0	1	1
1	1	1	1	1	1	1	0	0	0	1

## **CPSC 359 Assignment 2: Gray Code Up/Down Counter**

Kell Larson 30056026

### **3. Bonus Circuit Output Functions:**

Please see handwritten page 1 for circuit output functions. It will be the same as the original circuit.

### **4. Bonus Flip-flop Input Functions:**

Please see handwritten page 5 for flip flop input functions.

### **5. Bonus Implementation of Logic Diagrams:**

Please see handwritten page 6 of the report for implemented logic diagrams.